

20.1

$$q = 35 \text{ C}$$
$$t = 1.0 \times 10^{-3} \text{ s.}$$

$$\therefore I = \frac{q}{t} = \frac{35 \text{ C}}{1.0 \times 10^{-3} \text{ s.}} = 35,000 \text{ A.}$$

**NOTICE**

This material may be  
protected by copyright  
law (Title 17 U.S. Code)

20.5

$$R = 11\Omega$$

$$V = 240V$$

$$I = ?$$

Since  $V = IR$

$$I = \frac{V}{R} = \frac{240V}{11\Omega} = 21.8182A$$

Rounded to two significant figures,  $I = 22A$

20.11

$$\left. \begin{array}{l} I = 1200 \text{ A} \\ V = 1.6 \times 10^{-2} \text{ V} \end{array} \right\} R = \frac{V}{I} = \frac{1.6 \times 10^{-2} \text{ V}}{1200 \text{ A}} = 1.33 \times 10^{-5} \Omega$$

$$\begin{array}{l} \rho_{\text{Cu}} = 1.72 \times 10^{-8} \Omega \cdot \text{m} \quad (\text{from table \#1 in chapter 20}) \\ L = 0.24 \text{ m} \end{array}$$

$$\text{Since } R = \frac{\rho L}{A} \rightarrow A = \frac{\rho L}{R} = \frac{(1.72 \times 10^{-8} \Omega \cdot \text{m})(0.24 \text{ m})}{1.33 \times 10^{-5} \Omega} = 3.096 \times 10^{-4} \text{ m}^2$$

Because the cable is cylindrical, the cross-sectional area is

$$A = \pi r^2 \rightarrow r^2 = \frac{A}{\pi}$$

$$\therefore r = \sqrt{\frac{A}{\pi}} = \sqrt{\frac{3.096 \times 10^{-4} \text{ m}^2}{\pi}} = \boxed{9.9 \times 10^{-3} \text{ m}}$$

20.21

$$R = 24\Omega$$

$$V = 120V$$

$$P = ?$$

$$P = \frac{V^2}{R} = \frac{(120V)^2}{24\Omega} = \boxed{600W}$$

20.43

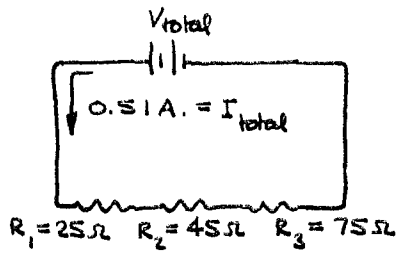


fig 1.

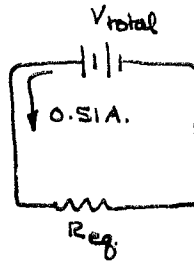


fig. 2.

a. For series resistors,  $R_{eq} = R_1 + R_2 + \dots$

$$\therefore R_{eq} = 25\Omega + 45\Omega + 75\Omega = \boxed{145\Omega}$$

b. Since series resistors pass the same current,  $I_1 = I_2 = I_3 = 0.51A = I_{total}$

$$\therefore V_1 = I_1 R_1 = (0.51A)(25\Omega) = 12.75V$$

$$V_2 = I_2 R_2 = (0.51A)(45\Omega) = 22.95V$$

$$V_3 = I_3 R_3 = (0.51A)(75\Omega) = 38.25V$$

The potential difference across all three resistors is the sum of the potential differences across each resistor:


$$V_{total} = V_1 + V_2 + V_3 = 73.95V \text{ or rounded to two significant figures}$$

$$V_{total} = \boxed{74V}$$

An alternate (and faster) way is suggested in Figure 2. From Ohm's law,

$$V_{total} = I_{total} R_{eq} = (0.51A)(145\Omega) = 73.95V \text{ or } \boxed{74V}$$

20.48

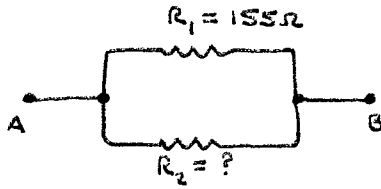

$$R_{AB} = R_{eq} = 115 \Omega$$

Since the equivalent resistance of parallel resistors is related by

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$

$$\frac{1}{R_2} = \frac{1}{R_{eq}} - \frac{1}{R_1} = \frac{1}{115 \Omega} - \frac{1}{1155 \Omega} = 2.24403 \times 10^{-3} \Omega^{-1}$$

$$\therefore R_2 = \frac{1}{2.24403 \times 10^{-3} \Omega^{-1}} = 445.625 \Omega$$

Rounded to three significant figures


$$R_2 = \boxed{446 \Omega}$$

20.49

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{16\Omega} + \frac{1}{8\Omega} = \frac{3}{16\Omega}$$

$$\therefore R_{eq} = \frac{16}{3}\Omega = \boxed{5\frac{1}{3}\Omega}$$

20.58

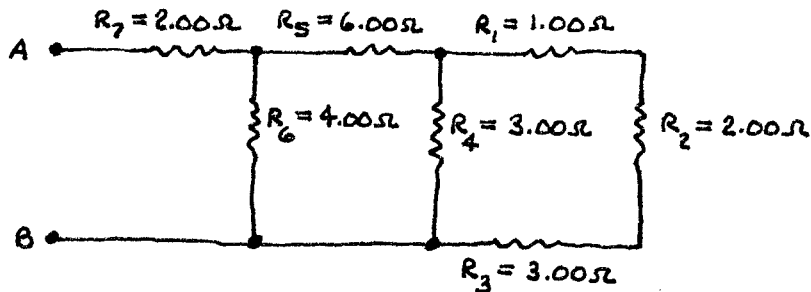

Replace  $R_1$ ,  $R_2$ , and  $R_3$  with  $R_8$ :

$$R_8 = R_1 + R_2 + R_3$$

$$R_8 = 1.00\Omega + 2.00\Omega + 3.00\Omega = 6.00\Omega$$



Replace  $R_4$  and  $R_8$  with  $R_9$ :


$$\frac{1}{R_9} = \frac{1}{R_4} + \frac{1}{R_8} = \frac{1}{3.00\Omega} + \frac{1}{6.00\Omega} = \frac{3}{6.00\Omega}$$

$$R_9 = 2.00\Omega$$



Replace  $R_5$  and  $R_9$  with  $R_{10}$ :
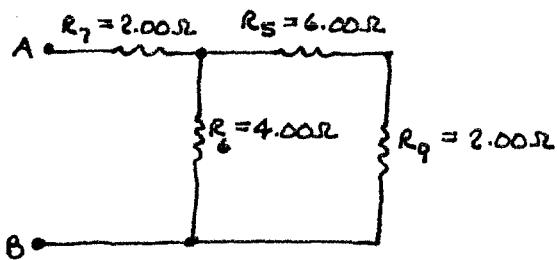
$$R_{10} = R_5 + R_9 = 6.00\Omega + 2.00\Omega = 8.00\Omega$$



Replace  $R_6$  and  $R_{10}$  with  $R_{11}$ :



$$\frac{1}{R_{11}} = \frac{1}{R_6} + \frac{1}{R_{10}} = \frac{1}{4.00\Omega} + \frac{1}{8.00\Omega} = \frac{3}{8.00\Omega}$$

$$R_{11} = \frac{8.00\Omega}{3} = 2.67\Omega$$




Replace  $R_7$  and  $R_{11}$  with  $R_{eq}$
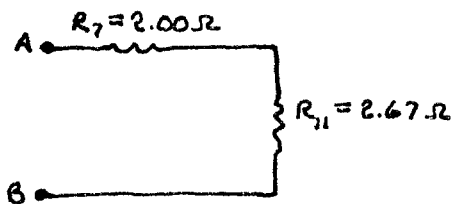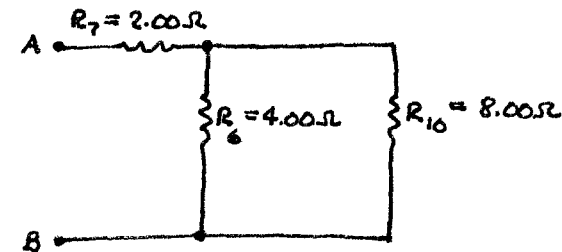
$$R_{eq} = R_7 + R_{11} = 2.00\Omega + 2.67\Omega = \boxed{4.67\Omega}$$



20.60

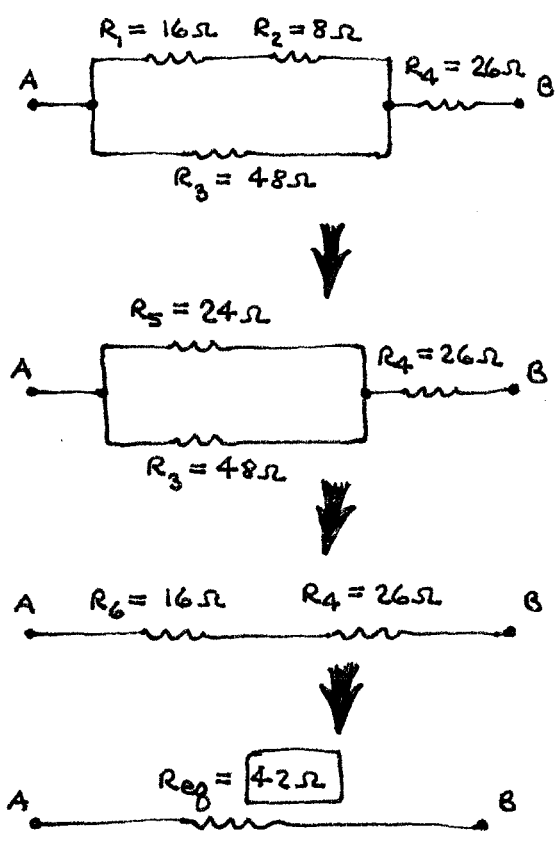

$$R_5 = R_1 + R_2 = 16\Omega + 8\Omega = 24\Omega$$




$$\frac{1}{R_6} = \frac{1}{R_3} + \frac{1}{R_5} = \frac{1}{48\Omega} + \frac{1}{24\Omega} = \frac{3}{48\Omega}$$

$$\therefore R_6 = \frac{48\Omega}{3} = 16\Omega$$

$$R_{eq} = R_6 + R_4 = 16\Omega + 26\Omega = 42\Omega$$

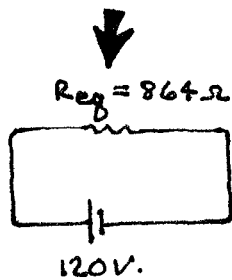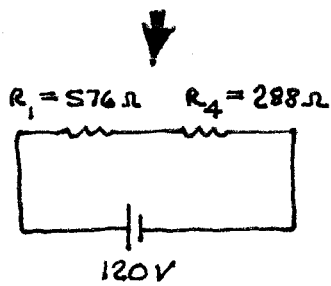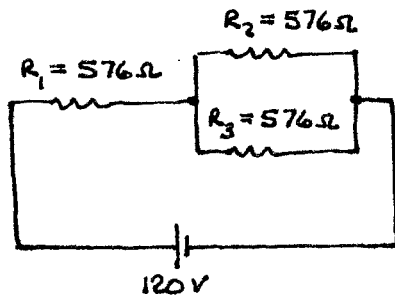20.64

Since  $P = \frac{V^2}{R} = I^2 R$ , to determine the power dissipated in each of the resistors shown below, we need only determine the current or the voltage associated with each resistor.



$$P_3 = \frac{V_3^2}{R_3} = \frac{(40V)^2}{576\Omega} = 2.777\dots W$$

$$\therefore P_2 = \frac{V_2^2}{R_2} = \frac{(40V)^2}{576\Omega} = 2.777\dots W$$

$$V_2 = V_3 = V_4 = 40V$$

$$\therefore V_4 = 40V.$$

$$\therefore V_4 = I_4 R_4 = (0.13888\dots A)(288\Omega)$$

$$\text{Also, } I_4 = I_{\text{total}} = 0.13888\dots A$$


$$\therefore P_1 = 11.1111\dots W$$

$$\therefore P_1 = I_1^2 R_1 = (0.13888\dots A)^2 (576\Omega)$$

$$I_1 = I_{\text{total}} = 0.13888\dots A$$
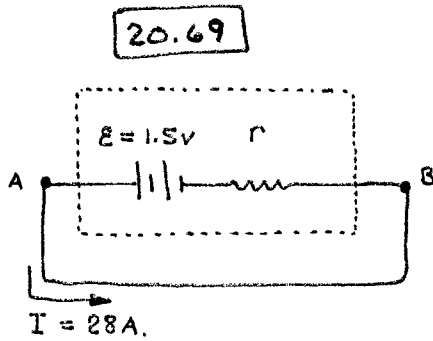
$$I_{\text{total}} = \frac{120V}{864\Omega} = 0.13888\dots A.$$





The electromotive force (emf),  $E$ , and the internal resistance,  $r$ , form the equivalent of a real battery. The terminals of the "real" battery are at A and B. When a "wire of negligible resistance" is placed between A & B, the current that flows in the circuit is limited by the internal resistance. According to Ohm's law,

$$r = \frac{E}{I} = \frac{1.5\text{V}}{28\text{A}} = \boxed{0.054\Omega}$$

20.100

$$V = 12 \text{ V.}$$

$$P = 33 \text{ W.}$$

$$R = ?$$

$$I = ?$$

$$\text{Since } P = \frac{V^2}{R} \rightarrow R = \frac{V^2}{P} = \frac{(12 \text{ V})^2}{33 \text{ W}} = 4.363636 \dots \Omega = \boxed{4.4 \Omega}$$

$$\text{Since } P = IV \rightarrow I = \frac{P}{V} = \frac{33 \text{ W}}{12 \text{ V}} = \boxed{2.8 \text{ A.}}$$